



Please note that the links in the PEARL logotype above are “live” and can be used to direct your web browser to our site or to open an e-mail message window addressed to ourselves.

To view our item listings on eBay, [click here](#).

To see the feedback we have left for our customers, [click here](#).

This document has been prepared as a public service . Any and all trademarks and logotypes used herein are the property of their owners.

It is our intent to provide this document in accordance with the stipulations with respect to “fair use” as delineated in Copyrights - Chapter 1: Subject Matter and Scope of Copyright; Sec. 107. Limitations on exclusive rights: Fair Use.

Public access to copy of this document is provided on the website of Cornell Law School at <http://www4.law.cornell.edu/uscode/17/107.html> and is here reproduced below:

## Sec. 107. - Limitations on exclusive rights: Fair Use

Notwithstanding the provisions of sections 106 and 106A, the fair use of a copyrighted work, including such use by reproduction in copies or phono records or by any other means specified by that section, for purposes such as criticism, comment, news reporting, teaching (including multiple copies for classroom use), scholarship, or research, is not an infringement of copyright. In determining whether the use made of a work in any particular case is a fair use the factors to be considered shall include:

- 1 - the purpose and character of the use, including whether such use is of a commercial nature or is for nonprofit educational purposes;
- 2 - the nature of the copyrighted work;
- 3 - the amount and substantiality of the portion used in relation to the copyrighted work as a whole; and
- 4 - the effect of the use upon the potential market for or value of the copyrighted work.

The fact that a work is unpublished shall not itself bar a finding of fair use if such finding is made upon consideration of all the above factors



# High-Power Audio Amplifiers

MANNIE HOROWITZ\*

As we increase the power output of an amplifier, we run into a whole new set of problems which are of importance to the designer and which must be solved properly and efficiently. Learn what these problems are and how they have been handled by one manufacturer.

**T**HE CURRENT TREND toward more reserve power from high-fidelity audio amplifiers, has led to the need for the exertion of more care in the design of the power and output stages. Poor design can lead not only to electrical component or tube failure within the amplifier, but may result as well in tweeter-voice-coil burn-outs when an unchecked supersonic, audio, or parasitic oscillation is present at the output.

## Output Tube Efficiency

There are several tube types capable of high power output. The European EL-34/6CA7 can deliver as much as 100 watts in push-pull pentode operation. The Tung-Sol 6550 can do the same. However, the EL-34 is more efficient, dissipating less heat within the tube for specific power outputs, than does the 6550.

The efficiency of an output tube is defined as

$$\frac{\text{AC power delivered to the load}}{\text{plate} + \text{screen} + \text{heater power dissipations}} \times 100\%$$

Table I compares the power dissipated at the quiescent conditions by both the EL-34 and the 6550, when operated so as to permit the delivery of 100 watts to the load. The EL-34 dissipates 26 per cent less power than does the 6550. Although both tubes are excellent and especially well designed for high power applications, economy in design tends to

\* 945 E. 26th St., Brooklyn 10, N. Y.

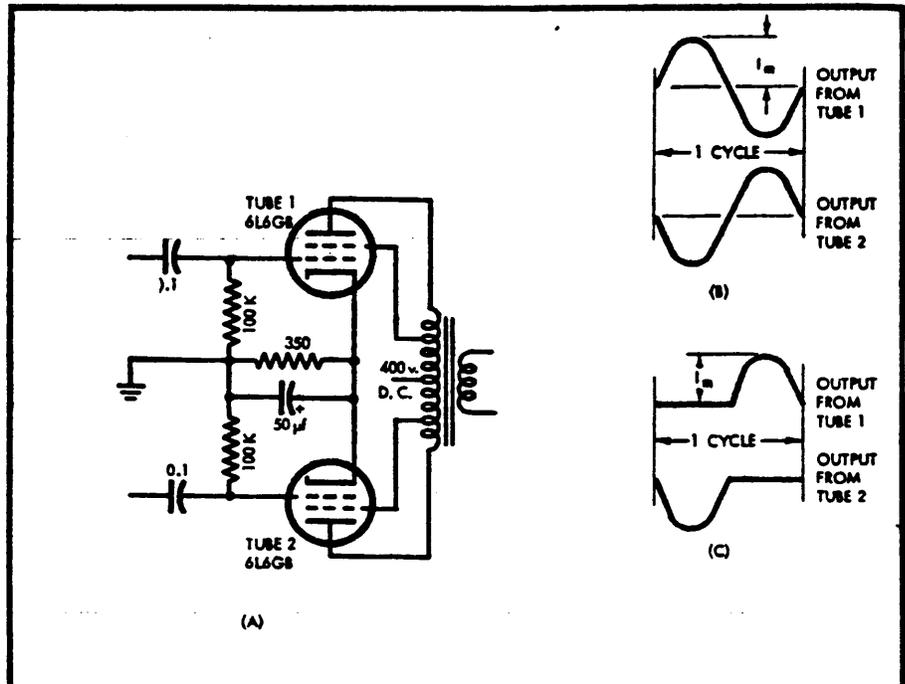


Fig. 1. (A) Schematic of typical Ultra-Linear push-pull output stage using 6L6GB tubes in Class AB. U-L tap is at 43% of turns from center on each side, or at 18.5% of total impedance. (B) Output over one cycle from each tube when biased for Class A operation. (C) Output from each tube if fixed bias is applied to obtain Class B operation.

indicate the use of the EL-34 rather than the 6550.

For clean, high power output, it is obvious to resort to push-pull operation. Maximum power considerations dictate the use of pentodes, but maximum curve

linearity for the low distortion necessary in high-fidelity amplifiers would suggest triode operation. However, the best compromise is accomplished with true Ultra-Linear circuitry, (A) in Fig. 1, where linearity equal to or better than triodes is achieved while at the same time delivering power outputs comparable with that of the pentodes.

Tests that I have run indicate that this method of operation permits raising the screen voltage about 20 per cent above the manufacturer's specifications without any injury to the output tubes. However, this should not be done if the screen power dissipation ( $E_{sc} \times i_{sc}$ ) or plate power dissipation ( $E_{pb} \times i_{pb}$ ) is higher than that recommended by the manufacturer. (Note: the above formulas for plate and screen dissipations are for fixed-bias applications only. When cathode bias is used, the plate and

TABLE I  
COMPARISONS BETWEEN 6550 and EL-34

	6550	EL-34/6CA7
Plate Dissipation	$600 \times 50 \times 10^{-6} = 30$	$800 \times 25 \times 10^{-6} = 20$
$E_{pb} \times i_{pb}$ watts	watts	watts
Screen Dissipation	$300 \times 1.5 \times 10^{-6} = 0.45$	$400 \times 4 \times 10^{-6} = 1.6$
$E_{sc} \times i_{sc}$ watts	watts	watts
Heater Power	$6.3 \times 1.8 = 11.4$	$6.3 \times 1.5 = 9.45$
$E_f \times i_f$ watts	watts	watts
Total Dissipation	41.85	31.05
per tube—watts	watts	watts

$E_{pb}$  = plate supply voltage  
 $E_{sc}$  = fixed cathode bias voltage  
 $E_{sc}$  = screen supply voltage  
 $E_f$  = filament voltage

$i_{pb}$  = zero signal plate current  
 $i_{sc}$  = zero signal screen current  
 $i_f$  = filament current



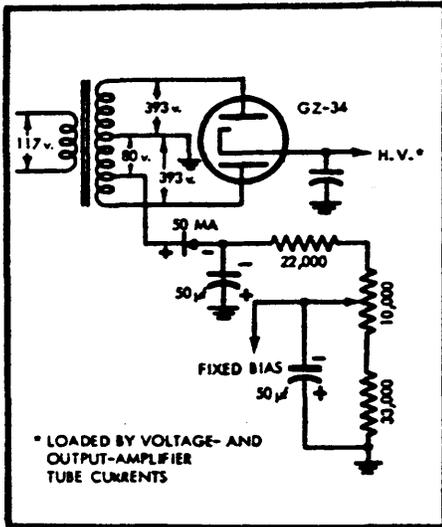


Fig. 4. Fixed bias supply voltage as used in amplifiers of Fig. 2. "Bias" pot adjusts bias voltage—for EL-34's, plate current should be 65 ma in this circuit.

of the excellent but low-efficiency speakers now on the market. To provide these additional impedances, the secondary of the transformer is tapped at points providing appropriate impedance ratios. Transformer manufacturers indicate in their specifications the impedance ratios supplied in their units.

The transformer used should also be capable of a wide-band flat frequency response to provide for stability in feedback circuits, as well as fidelity. The primary inductance must be high enough to prevent a rolloff of the low frequencies while the leakage inductance (theoretical equivalent inductance between the primary and secondary) must be low, not to allow rolloff at the high end of the audio-frequency spectrum. There must be sufficient high-grade steel laminations to permit a full-output power response down to the lowest audible frequency.

#### Power Supply

The power supply affects the response as well as the power output. The fixed bias (necessary in class B or class AB when operated close to class B) as well as the high voltage must provide good regulation. These voltages must remain reasonably constant over a large range of current variations to keep the output tubes working at their prescribed conditions for maximum output. Low rectifier and power-transformer-winding resistances help maintain the regulation. This same low impedance is necessary to retain the high output power at the low end of the audio spectrum.

There are many methods of obtaining the fixed bias. Manufacturers of amplifiers can have a transformer made with an extra winding for this purpose. The voltage at this winding is rectified, well filtered, and applied to the grids of the output tubes. Some commercial high

power amplifiers tap the high voltage winding as shown in Fig. 4.

Another method frequently used when special tapped transformers are not available employs a filament transformer in reverse. The 6.3-volt winding is connected across the filament winding on the main power transformer. Approximately 110 volts will then appear across the primary of the filament transformer. This 110 volts is rectified, filtered, and used to supply the bias for the output tubes as shown in Fig. 5. Although expensive, this method can be used by the

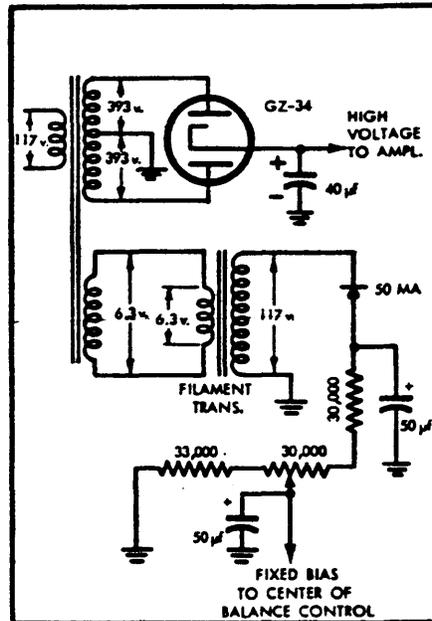


Fig. 5. Fixed bias supply using standard components.

amplifier builder without access to special transformers.

The high d.c. voltage shown in Figs. 4 and 5 is secured from a rectifier tube with a separate, rather than a filamentary type cathode. There is an important reason for this.

The filter capacitor used in this type of amplifier must be of the electrolytic type to conserve space. Oil-filled capacitors would require about six times the chassis area, providing no true advantage. Unfortunately, electrolytic capacitors are rated only at 500 working volts, with instantaneous peaks up to 575 volts. For longer life, the voltage applied to the capacitor should be kept within 500 volts. It should also be noted that the high voltage to be applied to the output tubes (such as the EL-34 under Ultra-Linear operation) is 470.

To fully understand why this requires the use of a rectifier with a separately heated cathode, it is only necessary to draw the equivalent circuit of a power supply. In Fig. 6, (A) shows the secondary of a power transformer supplying an a.c. voltage to the rectifier tube, which transforms the voltage into pulsating d.c. This in turn, is filtered to a

smooth voltage by the electrolytic capacitor,  $C$ , and applied to the load,  $R_L$ .

(B) shows the equivalent of the circuit in (A), with the transformer drawn as an inductance,  $L$ , and the applied a.c. voltage in series with the transformer winding resistance,  $R_t$ . The rectifier tube is shown as a unidirectional element in series with the plate resistance,  $R_p$ , of the tube. Since these resistive elements are in series with the rectifier, the equivalent circuit can take the form of (C) in Fig. 6.

As a theoretical example, let the rectified voltage,  $E_{dc} = 550$  volts,  $R_t = 100$  ohms,  $R_p = 200$  ohms, and the load resistance,  $R_L = 1720$  ohms. When this total resistance,  $R_t + R_p + R_L = 2020$  ohms is connected across the rectified d.c. voltage,  $E_{dc}$ , the current flowing is  $550 \text{ volts} / 2020 \text{ ohms}$ , or  $250 \text{ ma}$  ( $I = E/R$ ). When this current flows through  $R_t$  and  $R_p$ , the voltage drop through these resistors is  $250 \text{ ma} \times (100 + 200 \text{ ohms}) = 75 \text{ volts}$ . The voltage remaining across the load resistor,  $R_L$ , is then the total d.c. voltage, less the drop through  $R_t$  and  $R_p$ , or  $550 - 75 = 475 \text{ volts}$ . Since the load is

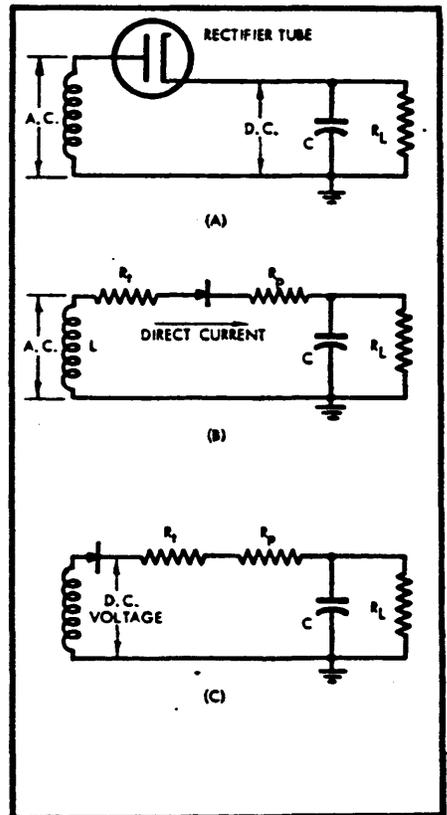


Fig. 6. (A) Power supply schematic. (B) Equivalent of (A), with transformer replaced by  $L$  and  $R_t$ , tube replaced by unidirectional element and plate resistance,  $R_p$ . (C) Positions of  $R_t$  and rectifier reversed, a permissible operation in a series circuit. When  $R_t$  is connected, direct current flow causes voltage drop in  $R_t$  and  $R_p$ .

in parallel with the filter capacitor, *C*, this 475 volts also appears across this capacitor. If the capacitor is rated at 500 volts, it will not break down.

Next, assume the same circuit as at (*C*) in *Fig. 6*; this time the load resistor, *R<sub>L</sub>*, is omitted. Since there is no completed d.c. circuit, no d.c. current flows; no flowing current means no voltage drop across *R<sub>i</sub>* and *R<sub>p</sub>*. Therefore the entire 550 volts appears across the filter capacitor, *C*, the open circuit for d.c. This 550 volts can easily damage a capacitor rated at 500 volts if kept there for a long period of time or applied frequently.

This is exactly what happens when there is no separately heated cathode in the rectifier tube.

A rectifier with a filament type cathode, such as the 5Y3G or the 5U4GB conducts at the moment the amplifier is turned on. The output tubes have not had the time to heat their cathodes so as to start conducting. Since there is no current being drawn from the high-voltage power supply for the first half to three-quarters of a minute, (while the output-tube cathodes are warming up) there is no current flowing through the power supply and rectifier tube. No flowing current means no voltage drop in the rectifier tube and power transformer (*Fig. 6*). All the high voltage then appears across the electrolytic capacitor, and this may damage it.

The solution to this problem is to prevent the rectifier from heating up fast and setting up a high voltage before the output tubes start conducting. A slow-heating, separate cathode will provide this necessary time delay to protect the electrolytic capacitors, while the output tube cathodes are heating up. This will prevent the initial excess voltage surge, protecting the capacitor.

Tubes like the 5V4G provide this feature. However, for higher current applications, as in high power amplifiers, either two 5V4G's are necessary or the European GZ-34 made by Mullard and Amperex, may be used.

#### Mechanical Considerations

There are several layout factors which must be carefully considered for a successful and durable amplifier.

The internal volume of tubes such as the EL-34 is small. It thus needs a large

ventilating area outside of the tube bulb to conduct away the excess heat. Tube manufacturers claim that the tube life of this (and any other tube) is an inverse function of the bulb temperature. They recommend that the maximum bulb temperature of 250° C should not be exceeded. (The bulbs of the tubes used in two EICO units were measured with Tempilac and did not exceed 230° C. under any enclosed conditions.)

To accomplish this, Mullard recommends as a rough approximation a distance of 40 millimeters or 1 9/16 in. between two tube bulbs and 30 millimeters or 1 1/8 in. between any tube bulb and any other component mounted on the chassis. These temperature specs should be carefully observed when using these or any other output tubes, although the distances between different types may vary. A good rule-of-thumb is one bulb diameter of space between tubes. However, this can vary considerably as in the case of the 6L6GB, 6550 and EL-84.

Power transformers should not be mounted close to the hot tubes. Although the transformer itself may have a low temperature, being placed too close to these tubes can raise the ambient temperature to such a degree that when added to the transformer's own temperature rise, the insulation can break down.

Another important consideration for a successful amplifier is the electrolytic capacitor. These components must run cool. At high temperatures (above 85° C. in some cases and above 65° C. in most instances) these capacitors may become excessively leaky. They may short out entirely, or ruin the rectifier tube. Electrolytic capacitors should not be mounted near hot components such as power output tubes and power transformers.

Ventilating slits or holes between and around hot tubes and transformers is a good method for cooling the components. These slits will provide a chimney effect, affording excellent ventilation. The bottom plate on the chassis should have similar holes and be raised from the actual mounting shelf to permit cool air to rise into the chassis. If a protective cover is used, this too should have enough open spaces to provide good ventilation. It should, however, be noted that good ventilation is no substitute for proper spacing of components. Æ